



PIPELINED ARITHMETIC AND LOGIC UNIT

Yash
18110080

Vrutik
18110191

Viraj
18110188

Vagisha
18110179

Shruti Gupta
18110163

CONCEPT

Objective

- Pipeline Arithmetic and Logic Unit to
- To improve the performance of CPU
 - Optimal use of hardware
 - Simultaneous execution of more than one instruction

Pipelining

- Division of the whole process into smaller operations, each taking place simultaneously
- Does not decrease time of operation. Instead, it increases the throughput
- All modern processors extensively use pipelining
Ex- Intel Core i7 (2nd generation) has 14 pipeline stages

Timing Diagram for Instruction Pipeline Operation

	Time													
	1	2	3	4	5	6	7	8	9	10	11	12	13	14
Instruction 1	FI	DI	CO	FO	EI	WO								
Instruction 2		FI	DI	CO	FO	EI	WO							
Instruction 3			FI	DI	CO	FO	EI	WO						
Instruction 4				FI	DI	CO	FO	EI	WO					
Instruction 5					FI	DI	CO	FO	EI	WO				
Instruction 6						FI	DI	CO	FO	EI	WO			
Instruction 7							FI	DI	CO	FO	EI	WO		
Instruction 8								FI	DI	CO	FO	EI	WO	
Instruction 9									FI	DI	CO	FO	EI	WO

- ☐ Assume equal duration
☐ reduce execution time for 9 instructions: 54 time units to 14 time units.

Methodology

- Hardware has divided into different stages to different stages perform different instructions at the same time
- Three-stage pipeline - IF/Decode, ALU, Write back stage
- Synchronized system - every task is completed on a clock tick
- Implementation of memory - managed by arrays
- Instruction and Data memory managed separately
- ARM7TDMI architecture followed

Operations and Opcodes

- | | |
|------------------------------|-----------------------|
| 1- AND (logic and) | 9 - TST(and w/o wb) |
| 2 - EOR (logic xor) | 10 - TEQ (xor w/o wb) |
| 3 - SUB (subtract) | 11 - CMP (sub w/o wb) |
| 4 - RSB (rev. sub) | 12 - CMN (add w/o wb) |
| 5 - ADD (add) | 13- ORR (OR) |
| 6 - ADC (add + carry) | 14 - MOV (operand 2) |
| 7 - SBC (sub with carry) | 15 - BIC (bit clear) |
| 8 - RSC (rev sub with carry) | 16 - MVN(~Operand 2) |
| | *wb - write back |

CODE


Stage 1 Instruction Fetch and Decode

- Task: Fetches the instruction from memory
- Control through Program Counter
- ARMv7 instruction format has been used

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0		
Condition Bits					0	1*	Opcode					S	Operand register 1					Destination register					Operand reg 2 / Immediate value										


Stage 2 Execute

- Implements 16 standard Data Processing Operations (defined in ARM 7)
- Updates the values of flags **nzcv** and **is_write**
- Checks for inter-dependent instructions
 - The operand value is read from the same register where the last instruction is storing the data
 - Solution - Direct value access for the next instruction
 - Conditional assignment of the operand value
 - Prevents bubbles in the process
 - Speeds up the process

 

Stage 3 Write Back

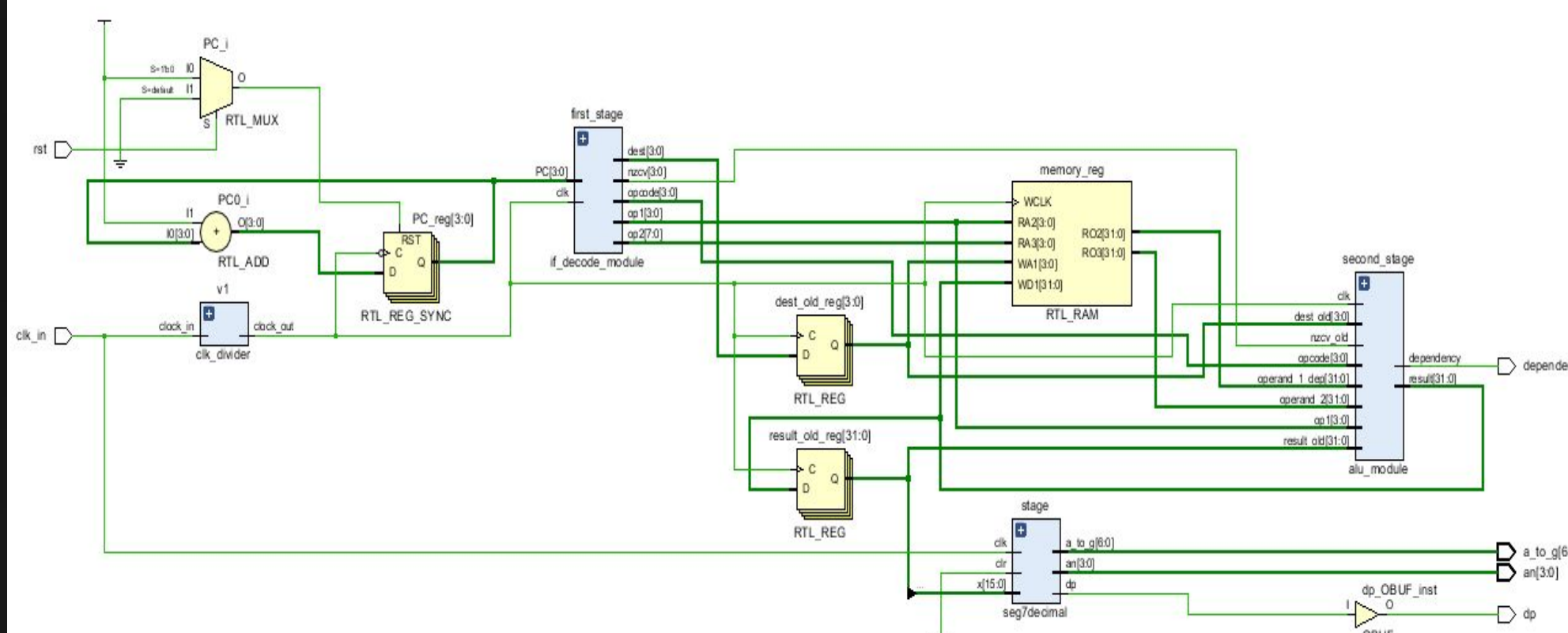- This is responsible for the memory write operation
- After the completion of the calculation stage - ALU execution
- To ensure there is no ambiguity (As update and read instructions are executed simultaneously)
 - Read at the negative edge of the clock
 - Write at the positive edge of the clock



Complete Pipeline RTL diagram


Pipelining Module

- The control module, which calls other modules
- Synchronises all other modules w.r.t. the clock
- Controls the Program Counter - increments as soon as the current instruction is executed
- Contains memory array - Memory read is performed from this module, without the clock tick
- Extra FFs - for result data and destination reg
 - result_old and dest_old
 - to prevent overwriting of variables

CONVERT


Simulation Output and Graphs

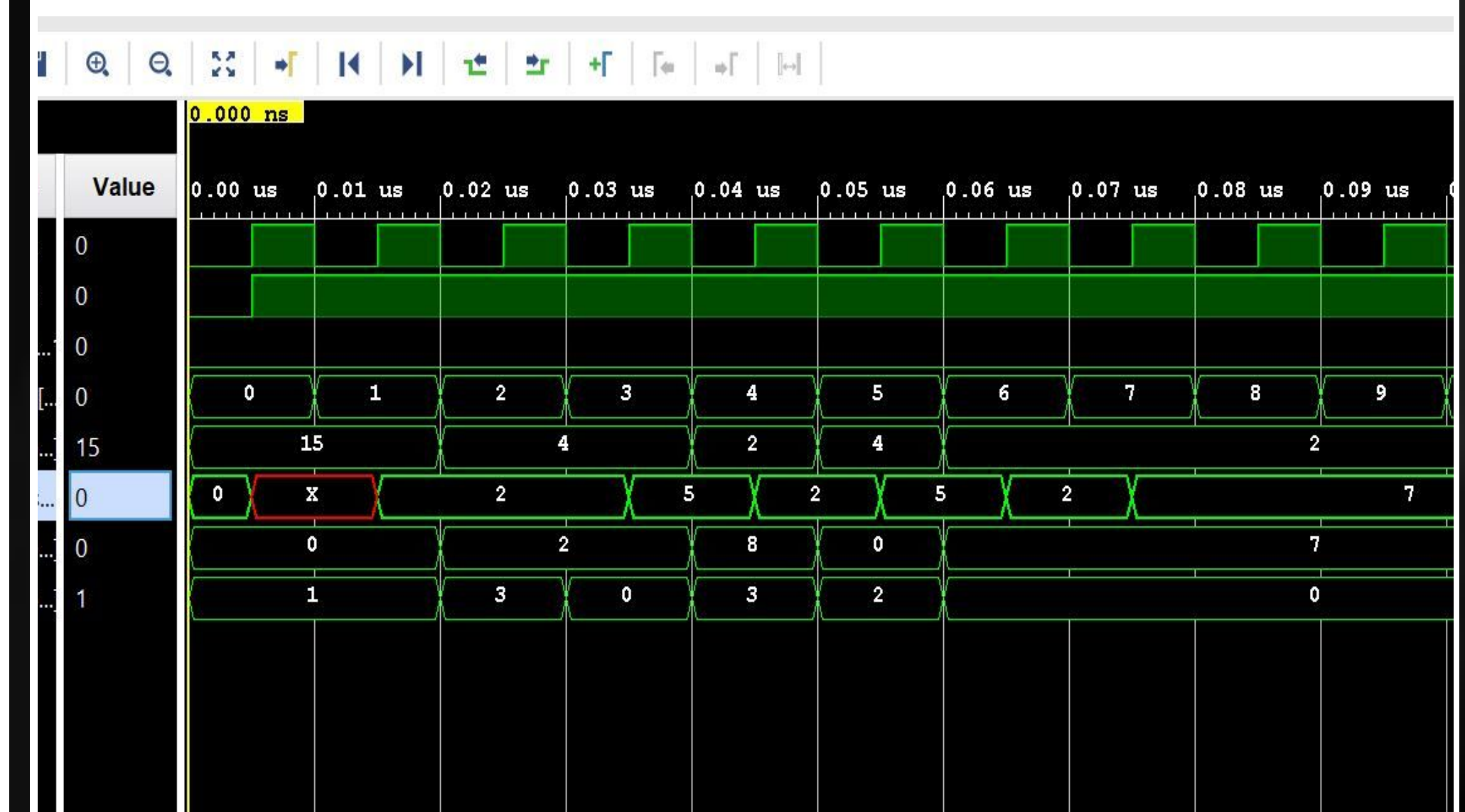- The first instruction is decoded in the first clock cycle
- The ALU executes the first instruction in the second cycle
- Meanwhile, the Instruction fetch stage works on the second instruction
- The pipelined ALU gives the first output in the third cycle
- Then, the system gives the output of consecutive instructions in consecutive clocks.



Implementation on Basys3 Board

 - The 32-bit instructions are stored in an array and stored on the FPGA.
- The pipelined ALU executes the instructions and shows the result on the FPGA board
- The 7-segment displays show the 16 least significant bits of the result
- The LED shows the dependency flag (5 - No dependency detected).



References

- [www.github.com/chsasank/ARM7](https://github.com/chsasank/ARM7)
- <https://github.com/kejriwalrahul/3-Stage-Pipeline>
- <http://vision.gel.ulaval.ca/~jflalonde/cours/1001/h17/docs/arm-instructionset.pdf>
- https://www.scs.tcd.ie/~waldroj/3d1/arm_arm.pdf
- <https://www.pantechsolutions.net/getting-started-with-arm-architecture>
- <https://github.com/mhyousefi/MIPS-pipeline-processor>
- <http://www.cs.cornell.edu/courses/cs3410/2012sp/project/pa1.html>